

Exercises: Boolean functions and logical circuits

Exercise 1. For the following Boolean functions of 3 variables, given by their tables of values, write the corresponding *canonical disjunctive form (CDF)* and *canonical conjunctive form (CCF)*. Using Veitch diagrams simplify the functions.

x	y	z	f_1	f_2	f_3	f_4	f_5	f_6	f_7	f_8
0	0	0	0	1	1	1	0	1	0	1
0	0	1	1	1	1	0	1	0	0	0
0	1	0	0	0	1	0	1	1	1	1
0	1	1	1	0	0	1	0	1	0	0
1	0	0	1	0	1	0	0	0	1	0
1	0	1	0	1	0	0	1	0	1	1
1	1	0	0	0	0	1	1	1	0	1
1	1	1	1	1	0	1	0	0	1	0

Exercise 2. Simplify the following Boolean functions of 4 variables using Veitch diagrams.

- $f_1(x_1, x_2, x_3, x_4) = x_1 \bar{x}_2 \bar{x}_3 \bar{x}_4 \vee x_1 x_2 x_3 \bar{x}_4 \vee x_1 x_2 \bar{x}_3 \bar{x}_4 \vee x_1 \bar{x}_2 x_3 \bar{x}_4 \vee x_1 \bar{x}_2 \bar{x}_3 x_4 \vee x_1 \bar{x}_2 x_3 x_4 \vee x_1 x_2 \bar{x}_3 x_4 \vee x_1 x_2 x_3 x_4$
- $f_2(x_1, x_2, x_3, x_4) = x_1 x_2 x_3 x_4 \vee x_1 x_2 x_3 \bar{x}_4 \vee x_1 x_2 \bar{x}_3 \bar{x}_4 \vee x_1 \bar{x}_2 \bar{x}_3 \bar{x}_4 \vee x_1 \bar{x}_2 x_3 \bar{x}_4 \vee x_1 \bar{x}_2 x_3 x_4 \vee x_1 x_2 \bar{x}_3 \bar{x}_4 \vee x_1 x_2 \bar{x}_3 x_4$
- $f_3(x_1, x_2, x_3, x_4) = x_1 x_2 x_3 x_4 \vee x_1 x_2 \bar{x}_3 \bar{x}_4 \vee x_1 x_2 \bar{x}_3 x_4 \vee x_1 \bar{x}_2 \bar{x}_3 \bar{x}_4 \vee x_1 \bar{x}_2 \bar{x}_3 x_4 \vee x_1 \bar{x}_2 x_3 \bar{x}_4 \vee x_1 \bar{x}_2 x_3 x_4 \vee x_1 x_2 \bar{x}_3 \bar{x}_4$
- $f_4(x_1, x_2, x_3, x_4) = x_1 \bar{x}_2 \bar{x}_3 x_4 \vee x_1 \bar{x}_2 \bar{x}_3 \bar{x}_4 \vee x_1 \bar{x}_2 x_3 \bar{x}_4 \vee x_1 \bar{x}_2 x_3 x_4 \vee x_1 x_2 \bar{x}_3 \bar{x}_4 \vee x_1 x_2 \bar{x}_3 x_4 \vee x_1 x_2 x_3 \bar{x}_4 \vee x_1 x_2 x_3 x_4$
- $f_5(x_1, x_2, x_3, x_4) = x_1 x_2 x_3 x_4 \vee x_1 x_2 \bar{x}_3 x_4 \vee x_1 x_2 \bar{x}_3 \bar{x}_4 \vee x_1 \bar{x}_2 \bar{x}_3 \bar{x}_4 \vee x_1 \bar{x}_2 \bar{x}_3 x_4 \vee x_1 \bar{x}_2 x_3 \bar{x}_4 \vee x_1 \bar{x}_2 x_3 x_4 \vee x_1 x_2 \bar{x}_3 \bar{x}_4$
- $f_6(x_1, x_2, x_3, x_4) = x_1 x_2 x_3 x_4 \vee x_1 x_2 \bar{x}_3 x_4 \vee x_1 x_2 \bar{x}_3 \bar{x}_4 \vee x_1 \bar{x}_2 \bar{x}_3 \bar{x}_4 \vee x_1 \bar{x}_2 \bar{x}_3 x_4 \vee x_1 \bar{x}_2 x_3 \bar{x}_4 \vee x_1 \bar{x}_2 x_3 x_4 \vee x_1 x_2 \bar{x}_3 \bar{x}_4$
- $f_7(x_1, x_2, x_3, x_4) = x_1 x_2 x_3 x_4 \vee x_1 x_2 \bar{x}_3 x_4 \vee x_1 x_2 \bar{x}_3 \bar{x}_4 \vee x_1 \bar{x}_2 \bar{x}_3 \bar{x}_4 \vee x_1 \bar{x}_2 \bar{x}_3 x_4 \vee x_1 \bar{x}_2 x_3 \bar{x}_4 \vee x_1 \bar{x}_2 x_3 x_4 \vee x_1 x_2 \bar{x}_3 \bar{x}_4$
- $f_8(x_1, x_2, x_3, x_4) = x_1 x_2 x_3 x_4 \vee x_1 x_2 \bar{x}_3 x_4 \vee x_1 x_2 \bar{x}_3 \bar{x}_4 \vee x_1 \bar{x}_2 \bar{x}_3 \bar{x}_4 \vee x_1 \bar{x}_2 \bar{x}_3 x_4 \vee x_1 \bar{x}_2 x_3 \bar{x}_4 \vee x_1 \bar{x}_2 x_3 x_4 \vee x_1 x_2 \bar{x}_3 \bar{x}_4$

Exercise 3. Using Karnaugh diagrams simplify the following Boolean functions given in CDF (disjunction of minterms):

$$\begin{aligned}
 f_1(x_1, x_2, x_3) &= m_0 \vee m_3 \vee m_4 \vee m_5 \vee m_6 \vee m_7; & f_2(x_1, x_2, x_3) &= m_1 \vee m_2 \vee m_4 \vee m_5 \vee m_6 \vee m_7; \\
 f_3(x_1, x_2, x_3) &= m_1 \vee m_2 \vee m_3 \vee m_4 \vee m_5 \vee m_7; & f_4(x_1, x_2, x_3) &= m_0 \vee m_1 \vee m_2 \vee m_3 \vee m_5 \vee m_6; \\
 f_5(x_1, x_2, x_3) &= m_0 \vee m_1 \vee m_2 \vee m_4 \vee m_6 \vee m_7; & f_6(x_1, x_2, x_3) &= m_0 \vee m_1 \vee m_3 \vee m_5 \vee m_6 \vee m_7; \\
 f_7(x_1, x_2, x_3) &= m_0 \vee m_1 \vee m_2 \vee m_3 \vee m_4 \vee m_7; & f_8(x_1, x_2, x_3) &= m_0 \vee m_2 \vee m_3 \vee m_4 \vee m_5 \vee m_6.
 \end{aligned}$$

Exercise 4. Simplify the following Boolean functions using Karnaugh diagrams.

- $f_1(x_1, x_2, x_3) = x_1(\bar{x}_2 \uparrow x_3) \vee \bar{x}_1 x_2$;
- $f_2(x_1, x_2, x_3) = x_3(x_1 \vee x_2) \vee (\bar{x}_2 \downarrow x_3)$;
- $f_3(x_1, x_2, x_3) = x_2(x_1 \uparrow \bar{x}_3) \vee \bar{x}_2 x_3$;
- $f_4(x_1, x_2, x_3) = x_1(x_2 \vee x_3) \vee (x_1 \downarrow \bar{x}_3)$;
- $f_5(x_1, x_2, x_3) = x_3(\bar{x}_1 \uparrow x_2) \vee x_1 \bar{x}_3$;
- $f_6(x_1, x_2, x_3) = x_2(x_1 \vee x_3) \vee (\bar{x}_1 \downarrow x_2)$;

$$7. \quad \overline{f_7(x_1, x_2, x_3)} = x_2(\overline{x_1} \uparrow x_3) \vee \overline{x_1 x_2}; \quad 8. \quad \overline{f_8(x_1, x_2, x_3)} = x_3(x_1 \vee x_2) \vee (\overline{x_1} \downarrow x_3).$$

Exercise 5. Using Quine's method simplify the following Boolean functions of 4 variables given by their values 1 :

$$\begin{aligned} f_1(1,1,1,1) &= f_1(1,1,0,1) = f_1(0,1,1,1) = f_1(1,1,0,0) = f_1(0,1,0,0) = f_1(0,0,0,0) = f_1(0,0,0,1) = f_1(0,0,1,1) = 1; \\ f_2(1,1,0,1) &= f_2(0,1,0,1) = f_2(0,1,0,0) = f_2(0,0,0,0) = f_2(0,0,1,0) = f_2(1,0,1,1) = f_2(1,0,0,1) = f_2(0,0,1,1) = 1; \\ f_3(0,1,0,1) &= f_3(0,1,0,0) = f_3(0,1,1,0) = f_3(1,0,1,0) = f_3(1,0,0,0) = f_3(0,0,1,0) = f_3(1,0,0,1) = f_3(0,0,0,1) = 1; \\ f_4(0,1,0,1) &= f_4(0,1,1,1) = f_4(1,1,1,0) = f_4(1,1,0,0) = f_4(0,1,1,0) = f_4(1,0,0,0) = f_4(0,0,0,0) = f_4(0,0,0,1) = 1; \\ f_5(1,1,1,1) &= f_5(0,1,0,1) = f_5(0,1,1,1) = f_5(1,1,1,0) = f_5(1,1,0,0) = f_5(1,0,0,0) = f_5(1,0,0,1) = f_5(0,0,0,1) = 1; \\ f_6(1,1,0,1) &= f_6(0,1,0,1) = f_6(0,1,1,1) = f_6(1,1,1,0) = f_6(0,1,1,0) = f_6(1,0,1,0) = f_6(1,0,1,1) = f_6(1,0,0,1) = 1; \\ f_7(1,1,1,1) &= f_7(1,1,0,1) = f_7(0,1,0,1) = f_7(0,1,0,0) = f_7(0,1,1,0) = f_7(0,0,1,0) = f_7(1,0,1,1) = f_7(0,0,1,1) = 1; \\ f_8(1,1,1,1) &= f_8(1,1,1,0) = f_8(1,1,0,0) = f_8(1,0,0,0) = f_8(0,0,0,0) = f_8(0,0,1,0) = f_8(1,0,1,1) = f_8(0,0,1,1) = 1. \end{aligned}$$

Exercise 6. Using Quine's method simplify the following Boolean functions given by their values 0.

$$\begin{aligned} f_1(0,1,0) &= f_1(0,1,1) = f_1(1,0,1) = 0; & f_2(0,0,0) &= f_2(0,0,1) = f_2(1,1,1) = 0; \\ f_3(0,0,1) &= f_3(0,1,0) = f_3(1,1,0) = 0; & f_4(0,0,0) &= f_4(0,1,1) = f_4(1,0,0) = 0; \\ f_5(0,0,0) &= f_5(1,1,0) = f_5(1,1,1) = 0; & f_6(0,1,0) &= f_6(1,0,0) = f_6(1,0,1) = 0; \\ f_7(0,1,1) &= f_7(1,0,0) = f_7(1,1,1) = 0; & f_8(0,0,1) &= f_8(1,0,1) = f_8(1,1,0) = 0. \end{aligned}$$

Exercise 7. Using Veitch-Karnaugh diagrams simplify the following Boolean functions of 4 variables.

$$\begin{aligned} 1. \quad f_1(x_1, x_2, x_3, x_4) &= x_1 x_4 \vee x_1 x_2 x_3 x_4 \vee \overline{x_1} x_2 x_4 \vee \overline{x_1} x_3 \vee x_3 x_4; \\ 2. \quad f_2(x_1, x_2, x_3, x_4) &= x_1 x_2 \vee \overline{x_1} \overline{x_2} x_3 x_4 \vee \overline{x_1} \overline{x_2} x_4 \vee \overline{x_1} x_3 \vee x_2 x_3; \\ 3. \quad f_3(x_1, x_2, x_3, x_4) &= x_1 x_4 \vee \overline{x_1} \overline{x_2} \overline{x_3} x_4 \vee \overline{x_1} \overline{x_2} x_4 \vee \overline{x_1} x_3 \vee x_3 x_4; \\ 4. \quad f_4(x_1, x_2, x_3, x_4) &= \overline{x_1} \overline{x_2} \vee x_1 x_2 \overline{x_3} x_4 \vee \overline{x_1} x_2 \overline{x_4} \vee \overline{x_1} x_3 \vee \overline{x_2} x_3; \\ 5. \quad f_5(x_1, x_2, x_3, x_4) &= \overline{x_3} x_4 \vee x_1 x_2 x_3 x_4 \vee \overline{x_3} x_2 x_4 \vee \overline{x_1} \overline{x_3} \vee \overline{x_1} \overline{x_4}; \\ 6. \quad f_6(x_1, x_2, x_3, x_4) &= \overline{x_1} \overline{x_4} \vee \overline{x_1} x_2 x_3 x_4 \vee x_1 x_2 x_4 \vee \overline{x_1} x_3 \vee \overline{x_3} x_4; \\ 7. \quad f_7(x_1, x_2, x_3, x_4) &= \overline{x_3} x_4 \vee \overline{x_1} x_2 \overline{x_3} x_4 \vee x_2 x_3 x_4 \vee x_1 x_3 \vee \overline{x_1} x_4; \\ 8. \quad f_8(x_1, x_2, x_3, x_4) &= x_3 x_4 \vee \overline{x_1} \overline{x_2} x_3 \overline{x_4} \vee \overline{x_2} \overline{x_3} x_4 \vee \overline{x_1} \overline{x_3} \vee \overline{x_1} x_4. \end{aligned}$$

Exercise 8. For each of the following Boolean functions do: draw the corresponding logical circuit using derived gates, simplify the function and draw the logical circuits associated to all simplified forms of the initial function using only basic gates.

$$\begin{aligned} 1. \quad f_1(x, y, z) &= x(y \oplus z) \vee y(x \oplus z) \vee x(\overline{y} \downarrow z) \vee (x \downarrow y) \overline{z}; \\ 2. \quad f_2(x, y, z) &= x(y \uparrow z) \vee \overline{x}(\overline{y} \oplus z) \vee y(\overline{x} \oplus z); \\ 3. \quad f_3(x, y, z) &= x(\overline{y} \oplus z) \vee y(\overline{x} \oplus z) \vee \overline{x}(\overline{y} \downarrow z) \vee (\overline{x} \downarrow y) z; \\ 4. \quad f_4(x, y, z) &= \overline{x}(y \uparrow z) \vee x(\overline{y} \oplus z) \vee \overline{y}(\overline{x} \oplus z); \\ 5. \quad f_5(x, y, z) &= \overline{x}(y \oplus z) \vee \overline{y}(x \oplus z) \vee \overline{x}(y \downarrow z) \vee (\overline{x} \downarrow y) \overline{z}; \\ 6. \quad f_6(x, y, z) &= x(\overline{y} \uparrow z) \vee \overline{x}(y \oplus z) \vee \overline{y}(\overline{x} \oplus z); \\ 7. \quad f_7(x, y, z) &= x(y \oplus \overline{z}) \vee y(\overline{x} \oplus z) \vee x(y \downarrow z) \vee (x \downarrow y) \overline{z}; \\ 8. \quad f_8(x, y, z) &= x(\overline{y} \uparrow z) \vee \overline{x}(\overline{y} \oplus z) \vee y(x \oplus \overline{z}). \end{aligned}$$

Exercise 9. Draw a logical circuit having 3 input wires and containing all basic and derived gates. Write the corresponding Boolean function, simplify it and then draw a simplified circuit equivalent with the initial circuit.

Exercise 10. Write a Boolean function of 4 variables given by its table of values, simplify it and draw the logical circuits corresponding to all its simplified forms.